

Lab 2

Power block verilog model

Systems On-Chip

Group nr.: 3

Student-ID-1: ist1112497 Kristian Guttormsen Gøystdal

Student-ID-2: ist1113000 Miki Tecle Hagos

Student-ID-3: ist1112548 Einar Bergslid

Electrical and Computer Engineering
IST-ALAMEDA

2024

1 Power block design

Based on the datasheet provided for the power block, we designed the power block like shown in [Listing 1](#). The power block will provide these calculated values based on the different input configurations for the battery charger. The selection of current is made using the control signals, **cc**, **tc** and **cv**, that are set in the control unit.

```
1      // Calculate forced battery current
2      if (cc) begin
3          rl_iforcedbat = rl_C * (0.502 * icc[7] + 0.251 * icc[6] +
4              0.1255 * icc[5] + 0.0627 * icc[4] + 0.0314 * icc[3] + 0.0157
5              * icc[2] + 0.0078 * icc[1] + 0.0039 * icc[0]);
6      end else if (tc) begin
7          rl_iforcedbat = rl_C * (0.502 * itc[7] + 0.251 * itc[6] +
8              0.1255 * itc[5] + 0.0627 * itc[4] + 0.0314 * itc[3] + 0.0157
9              * itc[2] + 0.0078 * itc[1] + 0.0039 * itc[0]);
10     end else if (cv) begin
11         rl_iforcedbat = (rl_vcv - rl_vsensbat) / rl_Rch;
12     end else begin
13         rl_iforcedbat = 0;
14     end
```

Listing 1: always block that monitors charging state

2 Simulations

When simulating the new power charger block using the provided testbench we get the results shown in [Listing 2](#). These values for the output current are close to the expected values for the given configurations for the battery and charger.

Listing 2: Console output from testbench of power block

```
cc=0, tc=0, cv=0, (cv_voltage=3,7V cc=0.2A tc=0,04A) output
current is: 0.000000 A
cc=1, tc=0, cv=0, (cv_voltage=3,7V cc=0.2A tc=0,04A) output
current is: 0.199200 A
cc=0, tc=1, cv=0, (cv_voltage=3,7V cc=0.2A tc=0,04A) output
current is: 0.039200 A
```

```
cc=0, tc=0, cv=1, (cv_voltage=3,7V cc=0.2A tc=0,04A) output
current is: 0.093250 A
Simulation complete via $finish(1) at time 400 NS + 0
```

In [Figure 1](#), we can see the simulation of the charger using the old power block and how the values look for each charging mode.

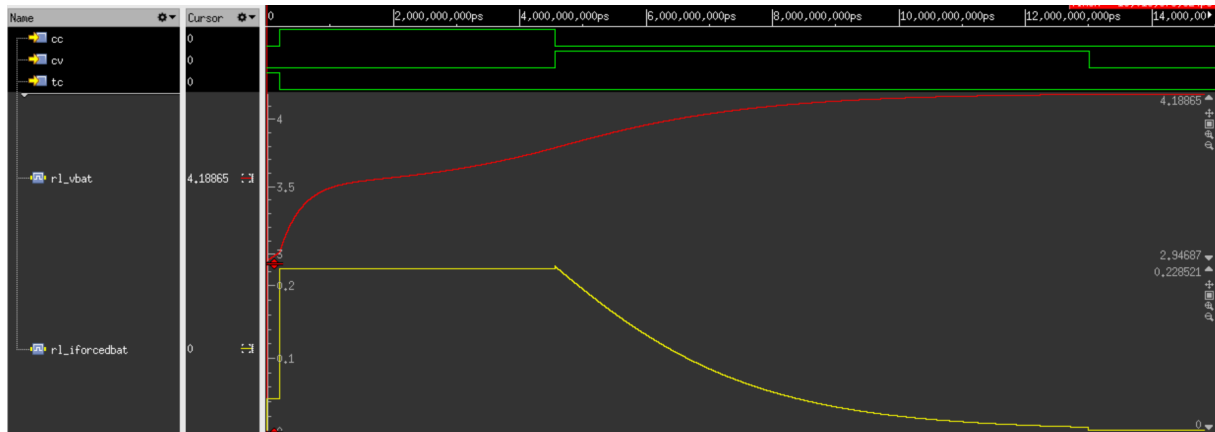


Figure 1: Current and voltage using old power block

This is how the charger with the new power block should look, with the correct current for each charging mode. If we compare [Figure 1](#) to [Figure 2](#), we can see that they share the same shape. The current value for the new power block is current reflected for each mode and the battery charges as expected.

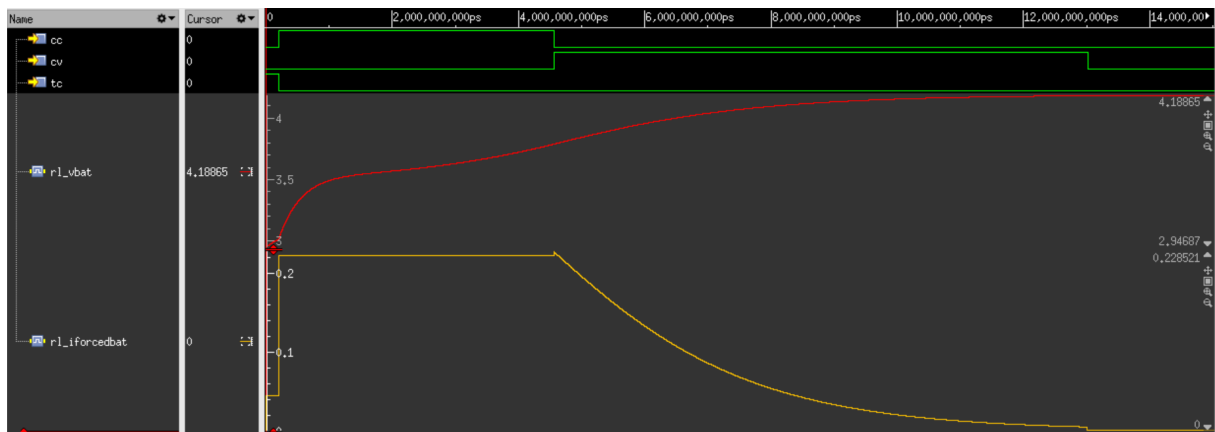


Figure 2: Current and voltage using new power block